

Due to 12/2020
zeyad hamza @ cet.edu.ly

Data acquisition

EE 463

(1)

18/11/2019

to Transfer information from Transducer to Controller
by changing the electrical signal to Digital.

1. RTD \rightarrow PT 100 \rightarrow Transducer for Temp. can read
[0 ~ 139 Ω]
@ $0^\circ\text{C} = 100 \Omega$, [0.39 $\Omega/^\circ\text{C}$]

Ex: @ $25^\circ\text{C} \Rightarrow 100 + (25 \times 0.39) = 108.97 \Omega$

TTL

CMOS

	0	1	0	1
	off	on	off	on
	0 volt	5 volt	0 volt	(3 ~ 18) volt
In \rightarrow	(0 ~ 0.8) V	(2 ~ 5.5) V		
out \rightarrow	(0 ~ 0.5) V	(4.4 ~ 5) V		

* 137 Ω what's The temp. $137 \Omega - 100 \Omega = 37 \Omega$
 $T = 37 \Omega / 0.39 \frac{\Omega}{^\circ\text{C}} = 94.87^\circ\text{C}$

10 \rightarrow Data acquisition: is The process by which physical phenomena from The real world are Transformed into electrical signals That are measured & converted into digital format for processing analysis & Storage by a Computer.

2. LM 35 \rightarrow Transducer for measure Temp.

(0 ~ 100 $^\circ\text{C}$) 10 mV/ $^\circ\text{C}$ [0 ~ 1 V]

1

(3)

أجيب AgiP

INTERNAL NOTES

Date

N 2

FROM 21/11/2019

TO


EE462

Your Ref

Our Ref

Subject

ذكرة
مراجعة
د/د

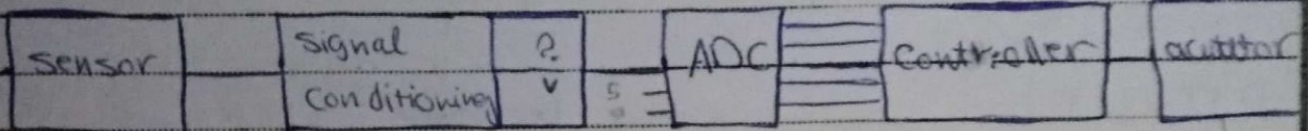

Fundamentals of Data acquisition

Sensor

Field wiring

Signal Conditioning → filtering, Amplification, isolation, linearization, etc.

Data acquisition hardware → ADC, DAQ cards, pre-amplifiers, etc.

Controller (operating system) → Arduino, PC, etc.

Data acquisition software

7805 → 5V , 7812 → , 7905 → -5V , 7912 → -

→ Voltage Regulation

Real Time Operating system → (RTOS) (Real Time Operating System)

25/11/2019


EE463

(3)


* Accuracy

تعريف - دقة قراءة الجهاز
ومقدار تقارب نتيجة القياس في الجهاز
Measurement Uncertainty - عدم اليقين

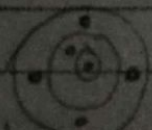
* Precision / Repeatability / Reproducibility




low precision
low accuracy

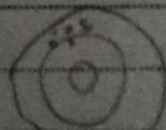

High Precision
low Accuracy

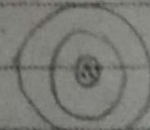



High accuracy
High Precision

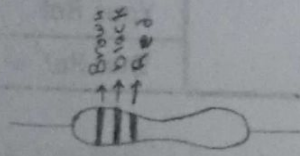

Resistor

(800 Ω ~ 1200 Ω)

★ linearity ▶

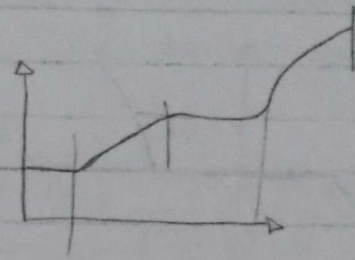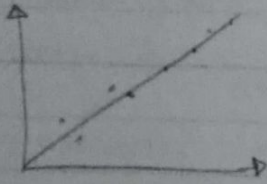

LM35 10mV/ $^{\circ}$ C

RTD @0 $^{\circ}$ C 100 Ω 0.39 Ω / $^{\circ}$ C

Example ▶

R(Ω)

Temp ($^{\circ}$ C)

307

200

7 Ω \leftarrow 30 $^{\circ}$ C ★

314

230

321

260

R=260.3 Ω \leftarrow T=0 $^{\circ}$ C ★

328


290

R_{T=0} = 261 Ω


$$\frac{200}{30} = 6.67$$

$$7 \times 6.67 = 46.67$$


$$307 - 46.67 = 260.3 \Omega$$

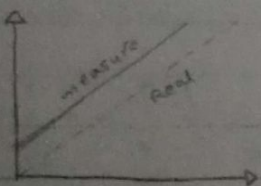

Bias zero drift

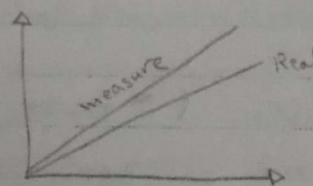


Sensitivity drift

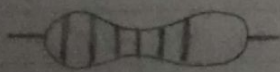

→ accuracy و آخر واحد علامه accuracy
Temp. coefficient


"Read it"

Masterpress

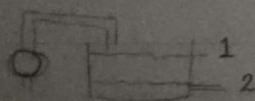

- حتى لما يوصل لمستوى معين يتوقف
المحرك عند المستوى (2) . آخر مستويين
مختلفين .

Agip		INTERNAL NOTES		Date	N
FROM	TO			Your Ref	Our Ref
Subject					

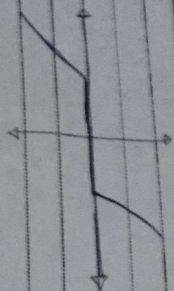

Resolution

28/NOV/2019

EE463

(4)

Range \rightarrow 500 (0 ~ 100)

Span \rightarrow 100 (100 ~ 100) = 100 - 0

Range \rightarrow -20 ~ 120

Span \rightarrow (120) - (-20) = 140

Signal Conditioning

RTD \rightarrow PT100 (100 Ω at 100 $^{\circ}\text{C}$)

D \rightarrow 100 Ω Sensitivity = 0.39 $\Omega/^{\circ}\text{C}$

EX \rightarrow (0 ~ 100 $^{\circ}\text{C}$) Temp range

(100 Ω + (0 $^{\circ}\text{C}$ \times 0.39 $\frac{\Omega}{^{\circ}\text{C}}$) \sim (100 Ω + (100 $^{\circ}\text{C}$ \times 0.39 $\Omega/^{\circ}\text{C}$)

(100 Ω \sim 139 Ω) #

EX \rightarrow (-20 $^{\circ}\text{C}$ \sim 120 $^{\circ}\text{C}$)

(100 Ω + (-20 $^{\circ}\text{C}$ \times 0.39 $\frac{\Omega}{^{\circ}\text{C}}$) \sim (100 Ω + (-7.8 Ω)

(92.2 Ω \sim 139 Ω) *

[4]

M35
Temp range
EX
accel

LM35

Sensitivity = $10 \text{ mV}/^\circ\text{C}$

Temp range ($0 \sim 100^\circ\text{C}$)


Sensor o/p range ($0 \text{V} \sim 1 \text{V}$)

EX

accelerometer range ($\pm 20g$), & @ $0g = 5 \text{mA}$
Sensitivity = 0.115 mA/g , calculate the sensor output range?

accelerometer range ($-20g \sim 20g$)
accelerometer range o/p $\rightarrow (5 + 20 \times 0.115)$
($2.7 \text{mA} \sim 7.3 \text{mA}$) #

5 EX

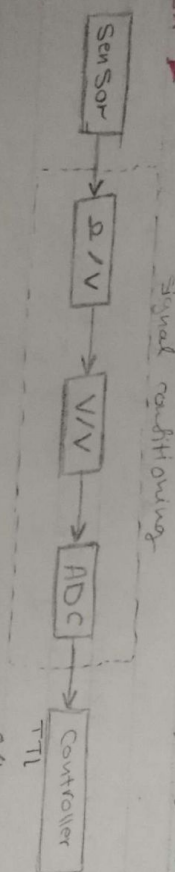


0/1
0/5
($0 \sim 0.8 \text{V}$) \sim ($2 \sim 5.5 \text{V}$)

PT100 range ($-20 \sim 80^\circ\text{C}$)

Sensor o/p range $\rightarrow [(-20^\circ\text{C} \times 0.39 \frac{^\circ\text{C}}{^\circ}) + 100] \sim [(80^\circ\text{C} \times 0.39 \frac{^\circ\text{C}}{^\circ}) + 100]$
($92.2 \sim 131.2 \Omega$)

* Single Ended

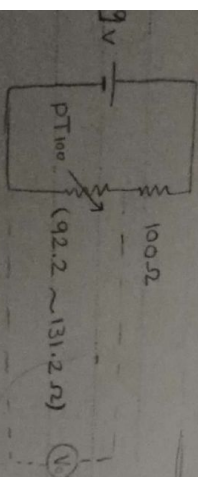

@ -20°C
@ 80°C

$$V_0 = 9 \text{V} \times \frac{92.2}{92.2 + 100} = 4.317 \text{V}$$

$$V_0 = 9 \text{V} \times \frac{131.2}{131.2 + 100} = 5.107 \text{V}$$

Voltage divider

Sensor output range in Voltage ($4.317 \text{V} \sim 5.107 \text{V}$)


FROM

TO

Your Ref

Our Ref

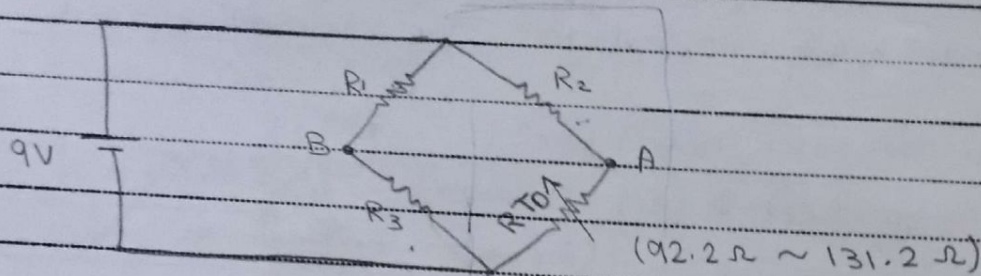Subject $R_1 = 120\Omega$, $R_2 = 130\Omega$, $R_3 = \text{calculate using } (*)$



1- more accuracy.

2- Start measuring from Zero. "best"

$$R_4 \cdot R_1 = R_2 \cdot R_3 \quad (*)$$

$$92.2 \cdot 120 = 130 \cdot R_3 \rightarrow R_3 = 85.107\Omega$$

$$V_A = 9 \times \frac{92.2}{92.2 + 130} = V_S \times \frac{R_1}{R_1 + R_2} = 3.734 \text{ V}$$

$$V_B = V_S \times \frac{R_3}{R_3 + R_1} = 9 \times \frac{85.107}{85.107 + 120} = 3.734 \text{ V}$$

$$\Delta V = V_A - V_B = 0 \text{ V}$$

$$V_B = 3.734 \text{ V}$$

$$V_A = 9 \times \frac{131.2}{131.2 + 130} = 4.52 \text{ V}$$

$$\Delta V = V_A - V_B = -0.786 \text{ V}$$

Bridge o/p Range (0 ~ 0.786 V) *

$$4.259 = 9 \times \frac{RTD + 130 \Omega}{110 \Omega - 100 \Omega}$$

$$\frac{110 \Omega - 100 \Omega}{0.39 \text{ A/C}^\circ} = 39.69 \text{ C}^\circ \quad \#$$



(5)

EE463

2/12/2019

EX ▶

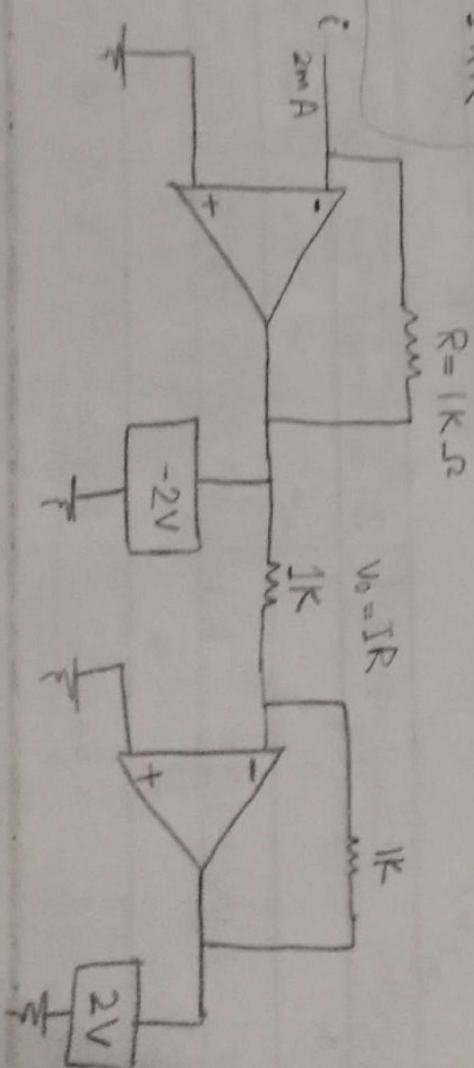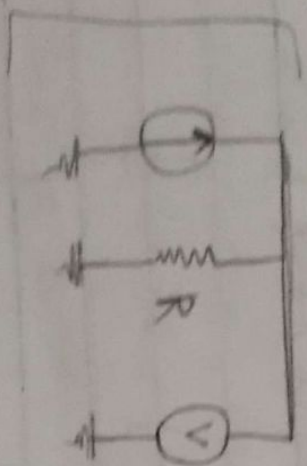Pressure sensor Sensitivity 0.12 mA/bar working in the Range $(0 \sim 40 \text{ bar})$, calculate the Sensor output Range



Agip آجيب

INTERNAL NOTES

Date

N

FROM

TO

Your Ref

Our Ref

Subject

0 ~ 150 bar

0 x 0.12 mA ~ 150 x 0.12 mA

(0 ~ 48 mA)

Using Resistance $R = 1k \Omega$

(0 ~ 4.8 mA x 1k)

0 ~ 4.8 V #

EX ▶

Pressure Sensor Sensitivity 0.11 mA/bar @ 2 bar
 0 bar = 27 mA, working in the range (1 ~ 15 bar)
 Calculate the sensor output range and convert it to voltage using $R = 500 \Omega$, calculate the voltage range.

Pressure Range (1 ~ 15 bar)

Sensor output Range $\left[\frac{1 \text{ bar} \times 0.11 \text{ mA}}{\text{bar}} + 27 \text{ mA} \right]$

$\left[\left(\frac{15 \text{ bar} \times 0.11 \text{ mA}}{\text{bar}} \right) + 27 \text{ mA} \right]$

$(2.81 \text{ mA} \sim 4.35 \text{ mA}) \times$

Voltage Range $(2.81 \text{ mA} \times 500 \Omega \sim 4.35 \text{ mA} \times 500 \Omega)$

$(1.405 \text{ V} \sim 2.175 \text{ V}) \#$

$(13.995 \text{ V} \sim 14.329 \text{ V}) \leftarrow$

EX ▶

LM35: Temp sensor working in the Range (0~100°C) with Sensitivity 10mV/°C, calculate the output sensor in the Range (25~40°C)

$$(25^{\circ}\text{C} \times \frac{10\text{mV}}{^{\circ}\text{C}}) \sim (40^{\circ}\text{C} \times \frac{10\text{mV}}{^{\circ}\text{C}})$$

$$(250\text{mV} \sim 400\text{mV})$$

accelerometer	MS1002	MS1002	MS1010	unit
Full Scale acceleration	±2	±5	±10	g
Scale Factor Sensitivity	1350	540	270	mv/g

$$V[t] = V[t-1] + ((A[t] + A[t-1]) * \frac{T}{2})$$

$$Pos[t] = Pos[t-1] + (A[t] + A[t-1]) * \frac{T}{2}$$

EX ▶

Using the accelerometer MS1010, calculate the acceleration, velocity, position, for each following Reading

interval = 100ms

Time	acc output (mV)	acceleration (g)	acceleration (m/s²)	V[t]	Displacement (m)	Position (m)
t0	0	0	0	0	0	0
t1	100mV	200/270 = 0.74g	0.74x9.81 = 7.26	0.363	0.018m	0.018m
t2	200mV	500/270 = 1.85g	18.167	1.634	0.118m	0.118m
t3	300mV	470/270 = 1.74g	17.07	3.395	0.218m	0.218m
t	400mV	200mV	0.74g			
	-120mV	-0.44g	-4.36			

أجيب AgIP

INTERNAL NOTES

Date

N

FROM

TO

Your Ref

Our Ref

Subject

$$V[t] = V[-1] + (A(t) + A(t-1)) * \frac{T}{2}$$

$$From \quad t = 200 \text{ ms}$$

$$V[t] = 0.363 + (18.167 + 7.26) 50 \times 10^{-3} = 1.634 \text{ m/s}$$

$$R_s[t] = 0.018 + (1.634 + 0.363) 50 \times 10^{-3} = 0.118$$

$$t = 300 \text{ ms}$$

$$V[t] = 1.634 + (17.07 + 18.167) 50 \times 10^{-3} = 3.395 \text{ m/s}$$

$$R_s[t] = 0.118 + (3.395 + 1.634) 50 \times 10^{-3} = 0.869 \text{ m/s}$$

$$t =$$

what's the sensor output Range?

Sensor acc Range $(-10 \text{ g} \sim +10 \text{ g})$

$$\text{a/p} \quad \left[\left(-10 \times \frac{270 \text{ m/s}^2}{\text{g}} \right) \sim \left(10 \times \frac{270 \text{ m/s}^2}{\text{g}} \right) \right]$$

$$(-2.7 \text{ V} \sim 2.7 \text{ V})$$


4/12/2019

FE463

(6)

operational Amplifier: OP AMP

① non-inverting Amp

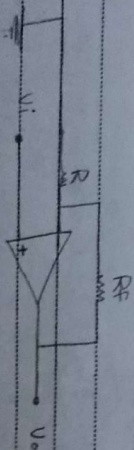


$$V_o = \left(\frac{R_f}{R_1} + 1 \right) V_i$$

EX ▶


$R = 1k\Omega$, $R_F = 1.5k\Omega$, $V_i = 1.75V$, $V_o = 4.375V$
 Same Fig above

2) Inverting Amp

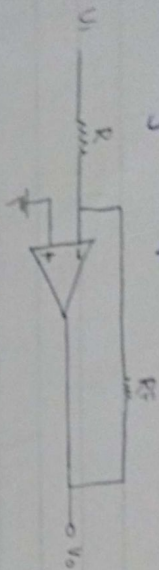


$$V_{o2} = -\frac{R_F}{R} \times V_i \quad \text{21}$$

12 EX ▶ 17/11/15/17/11

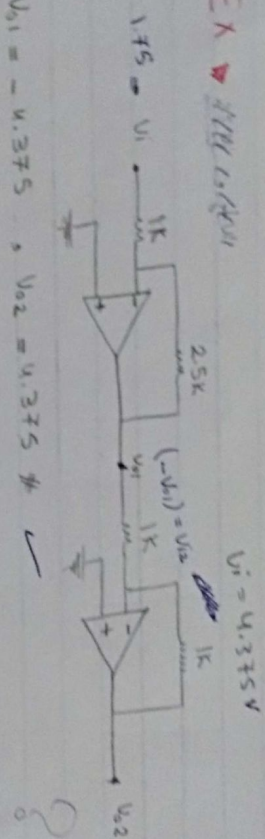

3) Addition

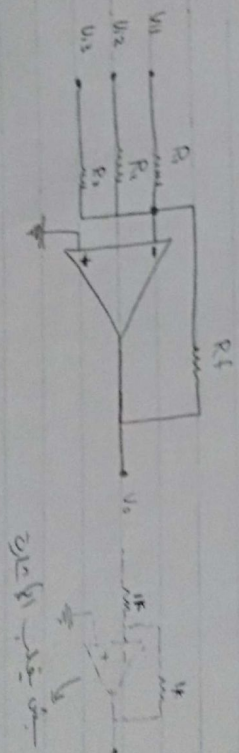

$$V_o = -\left(\frac{R_F}{R_1} V_{i1} + \frac{R_F}{R_2} V_{i2} + \dots + \frac{R_F}{R_n} V_{in}\right)$$

[11]

FROM

TO

Subject

Your Ref
Our Ref

EX ▶

$R_f = 2.5 \text{ k}\Omega$, $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$

$V_1 = 1.25 \text{ V}$, $V_2 = 0.75 \text{ V}$, $V_3 = 2 \text{ V}$, $V_o = ?$

$$V_o = 2.5 (1.25 + 0.75 + 2) = 10 \text{ V}$$


EX ▶

Find $2V_1 + 3V_2 + \frac{1}{4}V_3 = ?$

EX ▶ what's the average of the inputs?

$$\frac{1.25 + 0.75 + 2}{3} = \#$$

Subtractor ▶

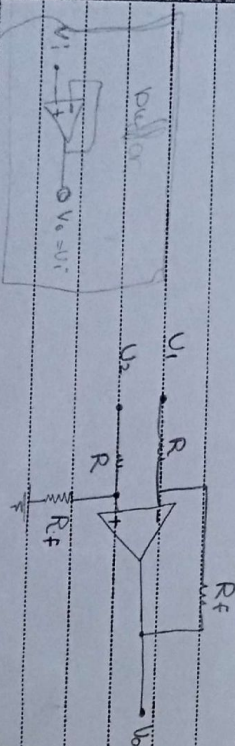


$$V_o = -\frac{R_f}{R} (V_1 - V_2)$$

EX ▶

RTD PT100 in the Range $(20^\circ\text{C} \sim 90^\circ\text{C})$, using

Wheatstone bridge, design circuit to which $R_1 = 120$, $R_2 = 125$, $V_s = 12 \text{ V}$, calculate the o/p voltage range from the bridge.

$$V_o = \frac{R_f}{R} (V_2 - V_1)$$

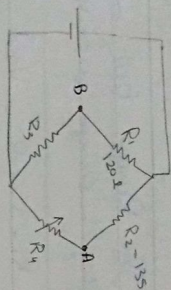

Temp Range = (20°C ~ 90°C)

Resistance Range [100 + (20 × 0.30)] ~ [100 + (90 × 0.30)]

(107.8 Ω ~ 135.1 Ω) #

$$R_1 R_1 = R_3 R_2$$

$$R_3 = \frac{R_1 R_1}{R_2} = \frac{107.8 \times 120}{135} = 95.82 \Omega \#$$

$$V_A = V_s \frac{R_1}{R_1 + R_2} = 5.3248 \text{ V} \#$$

$$\Delta V = V_A - V_B = 0 \checkmark$$


$$V_B = V_s \frac{R_3}{R_3 + R_1} = 5.3248 \text{ V} \#$$

@ 90°C

$$V_A = 12 \frac{135.1}{135.1 + 135} = 6.0622 \text{ V}$$

$$\Delta V = V_A - V_B = 0.67442 \text{ V}$$

Bridge o/p Range (0 ~ 0.67442 V)

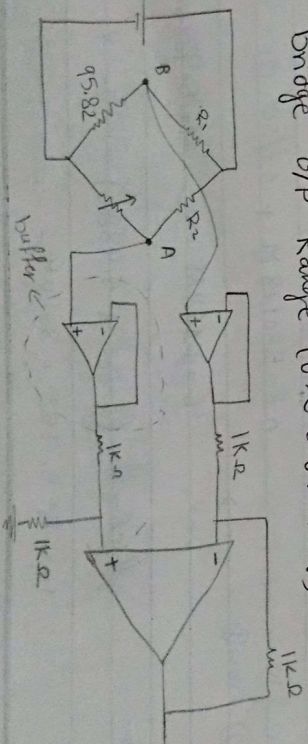

FROM

TO

Your Ref


Our Ref

Subject

EX ▶ using RTD-PT100 in The Range ($20^{\circ}\text{C} \sim 90^{\circ}\text{C}$)
design circuit to set o/p Voltage range ($0 \sim 4\text{V}$)?

using Voltage divider with $R_1 = 150\Omega$, $V_s = 12\text{V}$

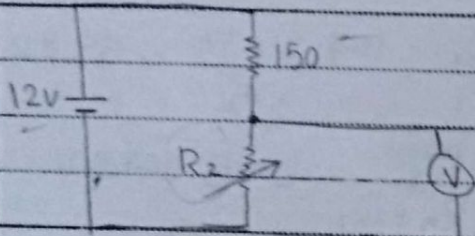RTD range ($107.81\Omega \sim 135.1\Omega$)



@ 20°C

$$V_o = 12 \times \frac{107.81}{107.81 + 150} = 5.018\text{V}$$

@ 90°C

$$V_o = 12 \times \frac{135.1}{135.1 + 150} = 5.686\text{V}$$

O/P range ($5.018\text{V} \sim 5.686\text{V}$)

$$V_o = V_i M + \text{offset}$$

$$4 = 5.686 M + \text{offset} \quad (1)$$

$$0 = 5.0178 M + \text{offset} \quad (2)$$

subtract (2) from (1)

$$4 = 0.668 M \Rightarrow M = 5.98802$$

$$\text{offset} = 4 - (5.686 \times 5.98802) = -36.04$$

$$V_o = V_i \cdot 5.982 - 30.04$$

أجيب أجيب

INTERNAL NOTES

Date


N

FROM

TO

Your Ref
Our Ref

Subject

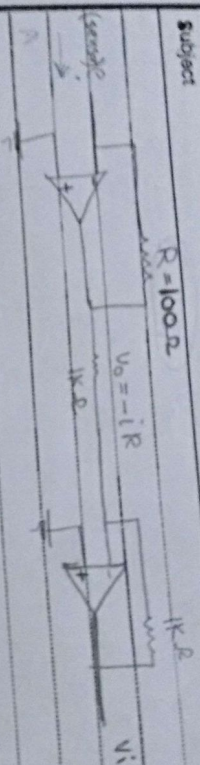

a/p Voltage Range $(10.4mA \times 100k \sim 28mV \times 100k)$
(1.04V ~ 2.8V)

* Add signal condition to convert from V to V

$$V_o = V_i \cdot M + offset$$

$$3 = 2.8M + offset \quad [1]$$

$$0 = 1.04M + offset \quad [2]$$

$$3 = 1.76M \quad [1-2]$$


$$M = 1.7045$$

$$offset = -1.04 \times 1.7045 = -1.7727$$

$$V_o = V_i \cdot 1.7045 - 1.7727$$

V_i	1.04	1.92	2.8
V_o	-0.00002	1.04994	2.9999

0 1.5 3

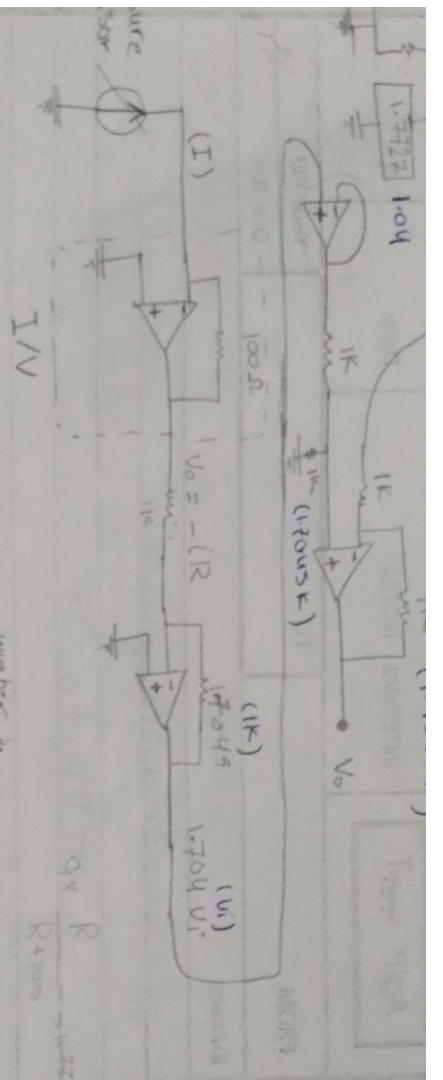

when you change eq, the sig change

$$\text{eg} \rightarrow [V_0 = 1.7045(V_i - 1.04)]$$

$$V_0 = 1.7045 V_i - 1.772$$

EX Pressure sensor sensitivity 12mV/bar
in the Range 10 ~ 20 bar & @ 0 bar = -15mV
Design signal conditioning ct for ADC which
Voltage Reference 10 ~ 5V

Pressure Range 10 bar ~ 20 bar

sensor o/p Range $(-15\text{mV} + (20 \times 12\frac{\text{mV}}{\text{bar}})) \sim -15\text{mV} + (240\text{mV})$

$(-15\text{mV} \sim 225\text{mV})$

no need for convert it is already Voltage o/p

$$V_0 = V_i M + \text{offset}$$

$$3 = 0.225 M + 0.88 \text{ Set } ①$$

$$0 = -0.015 M + 0.88 \text{ Set } ②$$

$$3 = 0.225 M \Rightarrow M = 12.5$$

0.1873

1.22

1.22

Agip آجيب

INTERNAL NOTES

Date

N

FROM

TO

Your Ref
Our Ref

Subject


$$V_{out} = 0.015 \times 12.5 = 0.1875V$$

$$V_o = 12.5V_i + 0.1875$$

V_i	-15mV	105mV	225mV
V_o	0	1.5	3

100% accuracy
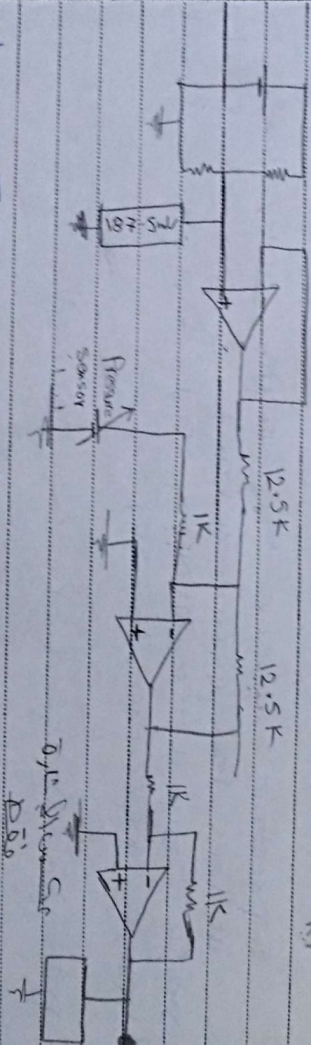
$$V_o = \left(\frac{R_f}{R_i} \right) V_i$$



what is the value of the pressure if the o/p voltage is 12V? (8 bar)
what is the o/p voltage if the pressure is 7 bar? (1.05V)

2019/Dec/12.

EEU63


(8)

EX ▶ Temp Sensor Sensitivity ($7.8 \text{ mV}/^\circ\text{C}$) working in The Range ($-20^\circ\text{C} \sim 80^\circ\text{C}$), Design S.C circuit for ADC with Reference range ($\pm 5\text{V}$)

Temp Range ($-20^\circ\text{C} \sim 80^\circ\text{C}$)

Sensor o/p range ($-20 \times 7.8 \frac{\text{mV}}{^\circ\text{C}} \sim 80 \times 7.8 \frac{\text{mV}}{^\circ\text{C}}$)

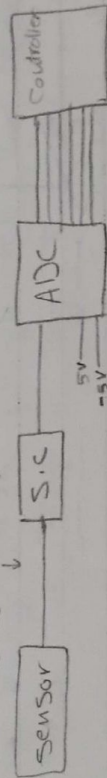($-156 \text{ mV} \sim 624 \text{ mV}$) *



$$V_0 = V_i M + \text{offset}$$

$$5 = 624 \times 10^{-3} M + \text{offset} \rightarrow \text{I}$$

$$-5 = -156 \times 10^{-3} M + \text{offset} \rightarrow \text{II}$$

$$10 = 0.78 M \rightarrow \text{I-II}$$

$$M = 12.8205 \#$$

$$\text{offset} = 5 - 624 \times 10^{-3} \times 12.8205$$

$$\text{offset} = -3 \#$$

$$V_0 = V_i \times 12.8205 - 3 \#$$

V_i	-0.156	0.234	0.624
V_0	-4.99998	-3 $\times 10^{-6}$	4.99992
	-5	0	5

→ "التحقق ضروري"

Agilp

INTERNAL NOTES

Date


N

FROM


TO

Your Ref
Our Ref

Subject

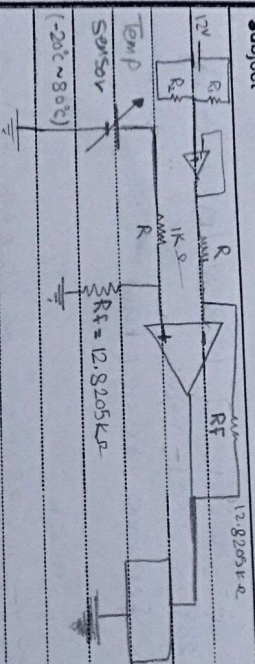

Comparator

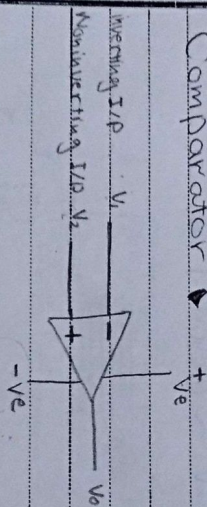


$$V_1 > V_2 \Rightarrow V_0 = -V_c$$

$$[V_2 > V_1 \Rightarrow V_0 = +V_c]$$

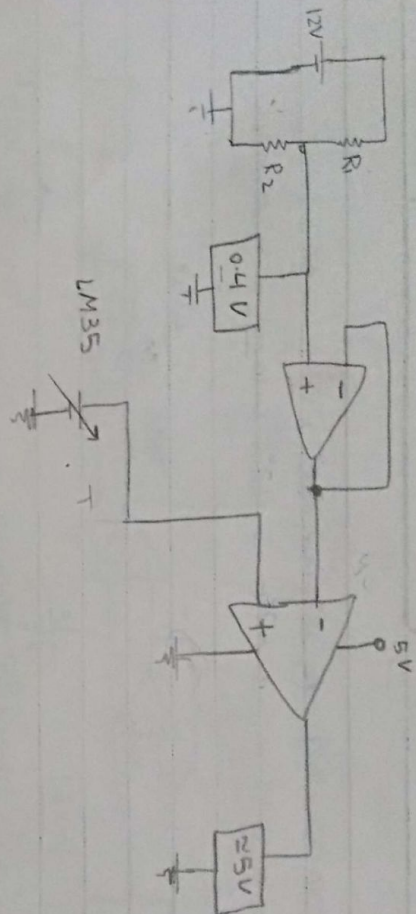
2) EX using LM35 Design Circuit that operate fan if the Temp is more than 40°C.

$$\text{Temp Sensor o/p @ } 40^\circ\text{C} = 40^\circ\text{C} \times \frac{10\text{mV}}{^\circ\text{C}} = 400\text{mV} \approx 0.4\text{V}$$



EX ▶ using LM 35 Design CT That operates heater if the Temp is less than 20°C . $T < 20^{\circ}$

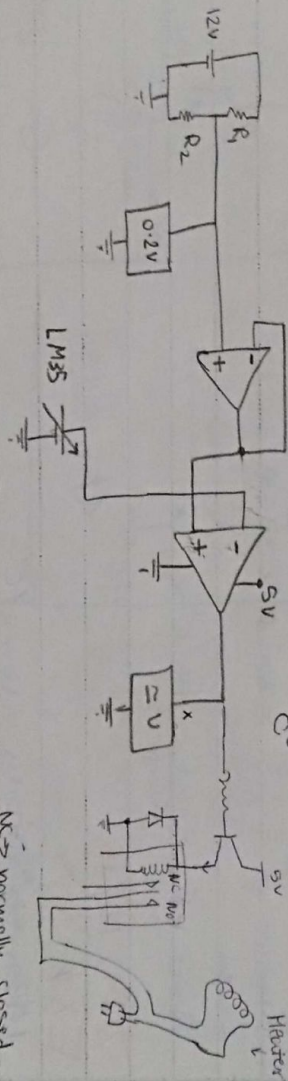Temp Sensor O/P @ $20^{\circ}\text{C} = 20^{\circ}\text{C} \times \frac{10\text{mV}}{^{\circ}\text{C}} = 200\text{mV}$



NC \rightarrow normally closed.
NO \rightarrow normally open.


EX ▶ using LM35 Design CT That operates Red led if the Temp is less than 18°C / blue led if the Temp is more than 42°C / Green led if the Temp is between $(18/42)$.

Good Sick

Subject	FROM	TO	Date	N

Temp sensor at $60^{\circ}\text{C} = 18^{\circ}\text{C} \times \frac{10\text{mm}}{^{\circ}\text{C}} = 180\text{mm}$

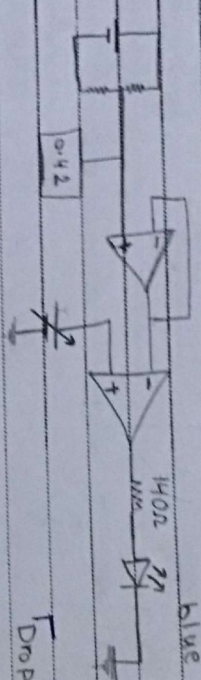22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100



Drop on bed

[illegible]

$$R_{\text{Red-LED}} = \frac{5-1.8}{10\text{mA}} = 320\Omega \approx 330\Omega \#$$

Blue-Red = 5-3.6
Wm A 140.2 #

2019/12/15

EE463

(9)

LM35, sensitivity = $10\text{mV}/^\circ\text{C}$

blue ice if Temp is more than 42°

Red 4 1/2 18

Green 11 between

So, we use way NAR Gate if The

blue & Red off Green Turn O.A.


pull up ^{high} until you're at zero \rightarrow NOIR

[illegible]


NOR $A \Rightarrow B \Rightarrow 1$

A	B	$f = A+B$
0	0	1
0	1	0
1	0	0
1	1	0

Example 11 of the MOS

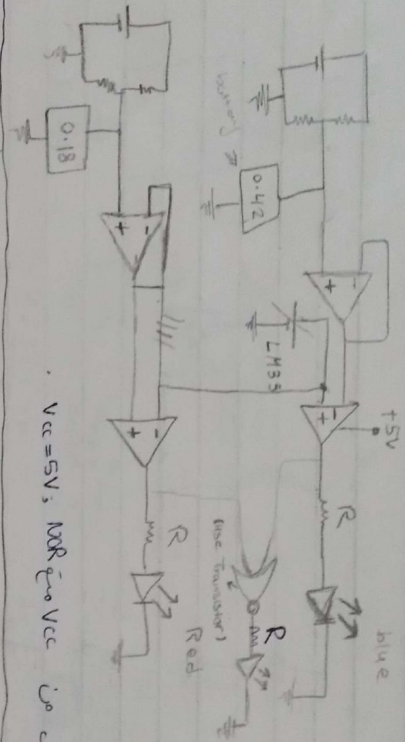


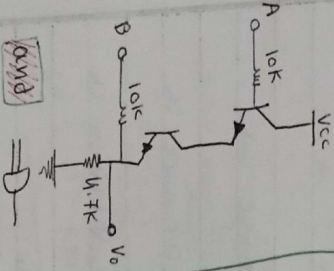$V_{CC} = 5V$; NOR gate V_{CC} is connected to R




AND $\Rightarrow D$


INVERTER

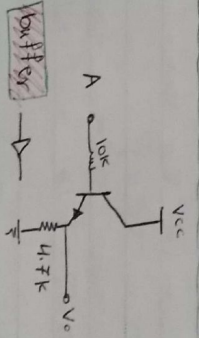

INVERTER $\Rightarrow D$

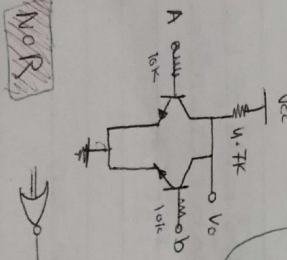


NOR $\Rightarrow D$

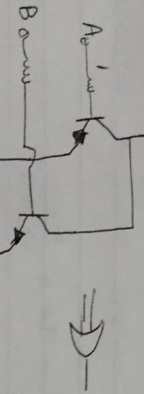

OR $\Rightarrow D$

Our Ref	Your Ref
---------	----------

FX Design Circuit Operator Release Value

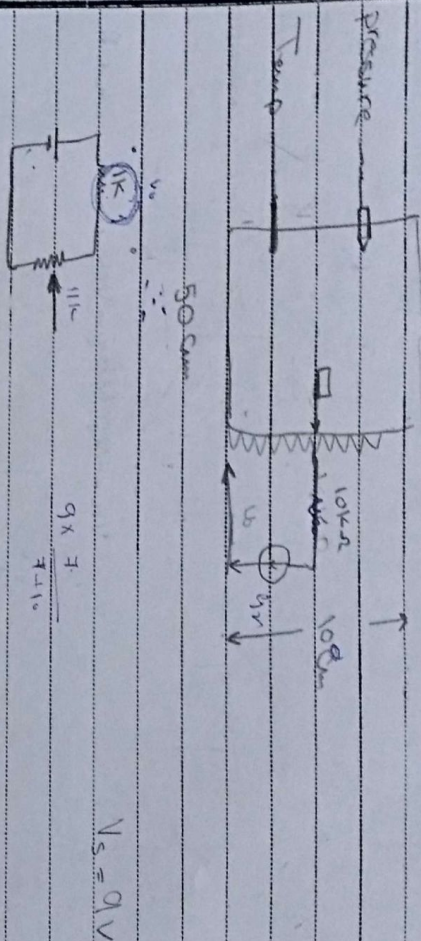

if the pressure is more than 10 bar (Release Value)
Red led if Temp is more than 50/pressure is
less than 2 bar.
or
what is the value of Vo if is set it is in
the Tank)

Pressure sensor sensitivity = 20 mV/bar

Volume = $\pi r^2 \times h = \pi \times (2.5)^2 \times 100 = 196350 \text{ cm}^3 = 196.35 \text{ L}$

Pressure sensor o/p at 10 bar $\rightarrow 10 \text{ bar} \times 20 \text{ mV} =$


$$VD = \frac{c \cdot 2 \cdot V}{R_2 + R_1} = 9 \text{ V}$$

Assume $R_1 = 1$ $K_R \rightarrow K_R$ less current cost

forward 500 20K when 20cm high
water

$$0.2 R_2 + (1K \times 0.2) = 9V R_2 \rightarrow R_2 = 22.7 \Omega \neq X$$

$$R_1 = 4.4K \quad R_2 = 100 \Omega$$

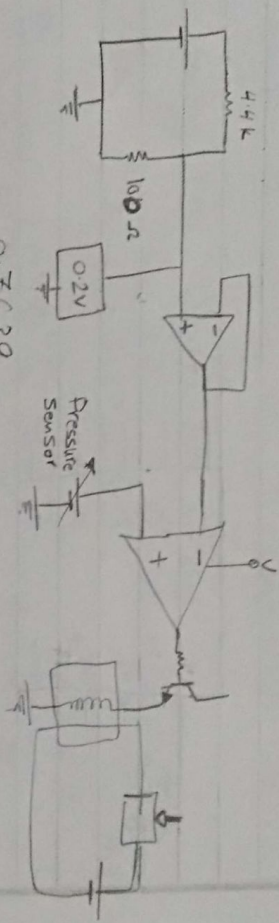

$$V_0 = 9V \times \frac{0.7639}{R_2}$$

$$\frac{1K + 101K}{21}$$

$$\pi r^2 \times h = 15000 \text{ cm}^3$$

$$= 2.68 \times 10^6$$

$$1000 \text{ cm}^3 \rightarrow 1L$$

$$h = 7.639 \text{ cm}$$

$$20 \text{ cm}$$

$$15L$$

$$0.7639K$$

$$2K$$

$$\frac{0.635}{10000}$$

$$V_0 = \frac{9 \times 7.639}{11K}$$

$$H > 80 \text{ cm} \quad \text{Led} \rightarrow \text{ON}$$

$$V_0 = 0.625$$

$$763.92$$

$$\frac{(+2)}{\text{volt}}$$

AgIP

INTERNAL NOTES

Date

N

FROM 2019/12/19

TO


EE463

Your Ref
Our Ref

10

Subject

Analogy to Digital Converter (ADC)

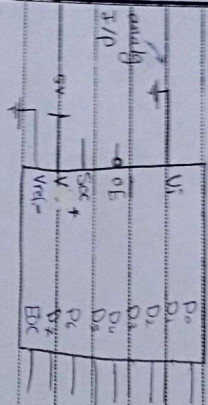

Unipolar (0~5V) / (-5~0V)

bipolar ($\pm 5V$), ($\pm 3V$)

OE \blacktriangleright output Enable

SOC \blacktriangleright Start of Conversion

Don't \blacktriangleright Digital I/P

EOC \blacktriangleright End of Conversion

$$\text{Resolution } (\Delta V) = \frac{V_{ref}^+ - V_{ref}^-}{2^n} = \frac{5}{2^8} = 19.53125 \times 10^{-3}$$

Digital O/P - analog I/P

ΔV

EX \blacktriangleright What is the digital O/P if the I/P is 1.85V?

$$\text{Digital O/P} = \frac{1.85}{19.53125 \times 10^{-3}} = 94.72 \approx 95$$

128 64 32 16 8 4 2 1
0 1 0 1 1 1 1 0

27 EX ▶ what's The analog I/P, if Digital O/P 01011000

$$\begin{aligned} \text{analog I/P} &= \text{Digital O/P} \times \Delta V \\ &= 88 \times 19.53125 \text{ mV} \\ &= 1.71875 \text{ V} \end{aligned}$$

28 EX ▶ using LM35D in The Range (20~115°C) design S.C Cct for (0~4V) Voltage Reference ADC:

- a] what is The digital O/P if The Temp (37°C, 107°C)
b] what is Temp if The digital O/P is (01010101)?

$$\text{Sensor O/P Range} (20 \times \frac{10 \text{ mV}}{^\circ\text{C}} \sim 115 \times \frac{10 \text{ mV}}{^\circ\text{C}})$$

$$(0.2 \text{ V} \sim 1.15 \text{ V})$$

$$V_o = m V_{in} + \text{offset}$$

$$0 = m \cdot 0.2 + \text{offset} \quad \text{①}$$

$$4 = m \cdot 1.15 + \text{offset} \quad \text{②}$$

$$\text{②} - \text{①} \quad 4 = m \cdot 0.95$$

$$m = 4.21052$$

$$\text{offset} = -0.8421$$

$$V_o = 4.21052 V_i - 0.8421 \text{ V}$$

FROM

TO

Your Ref
Our Ref


Subject

V_i	0.2	0.675	1.15
V_o	4 μ V	2.60005	3.99999

0 2 4

$$V_o = 4.21052 (V_i - 0.2) \quad \checkmark$$

4.21052 K

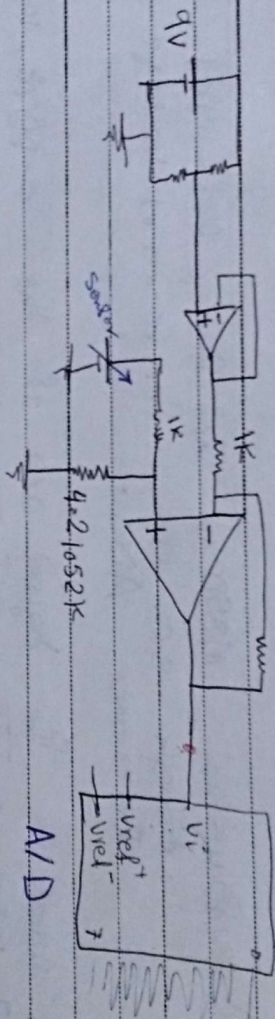

$$\Delta V = \frac{4V}{256} = 0.015625 V$$

$$\text{Digital o/p} = \frac{\text{analog IP}}{\Delta V} = \frac{28.682024}{0.015625}$$

@ 37°C

$$\text{Sensor o/p} = 37^\circ C \times 10 = 370 \text{ mV}$$

$$V_o = 4.21052 (0.37 - 0.2) = 0.7158 V$$

$$\text{Digital o/p} = \frac{0.7158}{0.015625} = 45.8107 \approx 45$$

$$\begin{pmatrix} 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ 0 & 0 & 1 & 0 & 1 & 1 & 0 & 1 \end{pmatrix}_2 \quad \#$$

② 107°C

$$\text{Sensor O/P} = 107^\circ\text{C} \times 10\text{mV} = 1.07\text{V}$$

$$V_0 = 4.2105 (1.07) - 0.8421 = 3.663135\text{V}$$

$$D_0 = \frac{3.663135}{0.015625} = 234.44 \approx 234$$

$$\begin{pmatrix} 128 & 64 & 32 & 16 & 8 & 4 & 2 & 1 \\ 1 & 1 & 1 & 0 & 1 & 0 & 1 & 0 \end{pmatrix}_2 \quad \#$$

$$\begin{pmatrix} 0 & 1 & 0 & 1 & 0 & 1 \end{pmatrix}_2 = (85)_2$$

$$\text{analog I/P} = 1.328125$$

$$1.328125 = 4.2105 V_i - 0.8421$$

$$V_i = 0.51543\text{V}$$

$$T = 0.51543 / 10\text{mV}$$

$$51.54^\circ\text{C}$$

~~XXXXXXXXXXXX~~

Agip أجيب

INTERNAL NOTES

Date

N

FROM 23/12/2019

TO

EE463

Your Ref
Our Ref

Subject EX

using Accelerometer which Sensitivity 10-15 mV/g
at $I_g = 1.9 \text{ mA}$ in the Range $\pm 15g$ design Signal
Condition cct for $\pm 3V$ Voltage reference $R = 300 \Omega$.

for digital o/p (unipolar) = analog I/P

$$\Delta V = \frac{V_{ref}^+ - V_{ref}^-}{2^n} = 0.02344 \Delta V$$

input

output

Shift register capability

-3

0000 0000

1111 1111 $\rightarrow 255 \rightarrow 2^8 = 255$

-3 + $\Delta V = -2.976$

0000 0001

EA \rightarrow analog I/P = 1.5 V

-3 + $\Delta V = -2.933$

0000 0010

$\frac{1.5+3}{23 \cdot 43 \times 10^{-2}} = 192$

analog I/P = 0 $\rightarrow 255/2 = 128$


Digital o/p (bipolar) = analog I/P + V_{ref}

ΔV

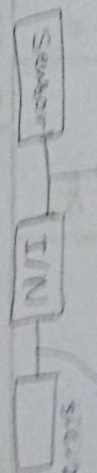a) what is the digital o/p if the I/P is 3.89 (15)
b) what is the acceleration if the digital o/p
(1001 0010)₂ $\rightarrow (146)_{10}$

$$\frac{\text{analog} + V_{ref}^+}{\Delta V} = 146$$

$$\text{analog} + V_{ref}^+ = 3.421 \rightarrow \text{analog} = 0.421$$



Range (15g ~ -15g)

Range O/P Sensor (-0.55 ~ 0.35 mA)

O/P Voltage (-0.11V ~ 0.67V)

$$V_o = M V_i + \text{offset}$$

$$3 = 0.67 M + \text{offset}$$


$$-3 = -0.11 M + \text{offset}$$

$$M = 7.6923, \text{offset} = -2.1538$$

$$V_o = 7.6923 (V_{in} - 0.27999)$$

$$V_o = 7.6923 V_{in} - 2.1538$$

V_i	-0.11	0.28	0.67V
V_o	2.499	4.499	3.000V

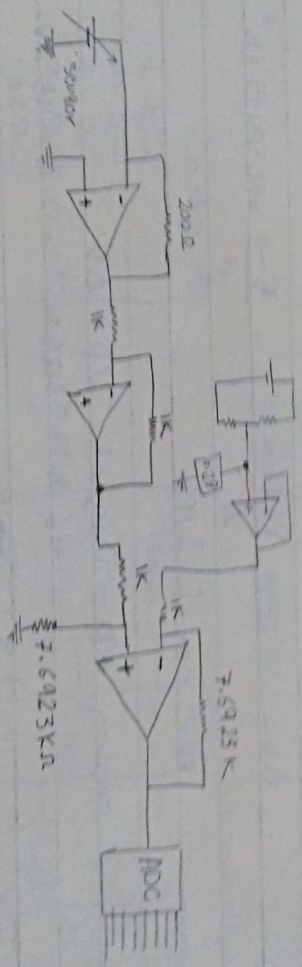

$$\Delta = 0.023437$$

$$\text{Digital O/P} = \frac{\text{analog} + V_{ref}}{\Delta V}$$

$$-3.8 \rightarrow 0.494 \text{ mA} \rightarrow 0.494 \times 200 \sim -98.8 \text{ mV} =$$

$$-0.0988 \text{ V} \rightarrow V_o = 7.6923 \times (-0.0988) - 2.1538$$

$$V_o = -2.91344$$

$$\text{Digital O/P} = 3.67448$$

0000 0106
1011 1111

FROM 26 /12/2019


TO EE462

Your Ref
Our Ref 12

Subject

Digital to Analog Converter

Digital I/P

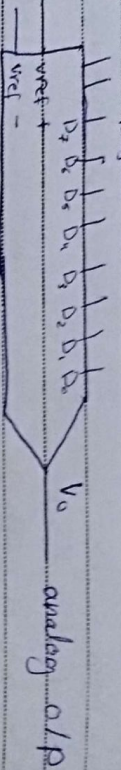


EX: what is the value of analog O/P if the digital I/P is $(101110)_2$ & the voltage Reference is between $(-5V)$?

$$\Delta V = \text{Voltage Reference} = \frac{5-0}{2^8} = 19.53125 \times 10^{-3}$$

$n = \text{No. of I/P}$

$$\text{EX: analog O/P} = \text{Digital I/P} \times \Delta V = 46 \times 19.53125 \times 10^{-3} = 0.8984375 V$$

Q1: EX: $01101101 \rightarrow$

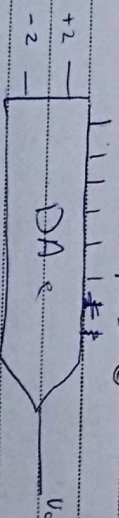


$$\text{Q2: } \Delta V = \frac{4}{2^6} = 0.0625 V$$

$$\text{① } = (27 \times 0.0625) - 2 = -0.3125 V$$

$$\text{② } = (53 \times 0.0625) - 2 = 1.3125 V$$

$$\text{Digital I/P} \times \Delta V - V_{ref} = \text{analog O/P}$$



Data Selector

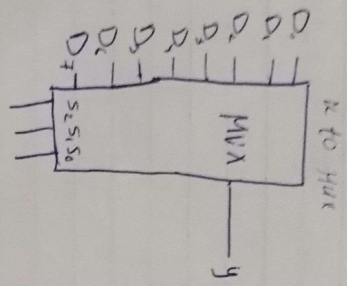

0 1 2 3 4 5 6 7
1 0 1 1 0 1 0 0
 S_2, S_1, S_0
1 1 0
 $y = D_6$ "

CMOS
 $0 \triangleq \text{Ground}$
 $5 \triangleq 1$

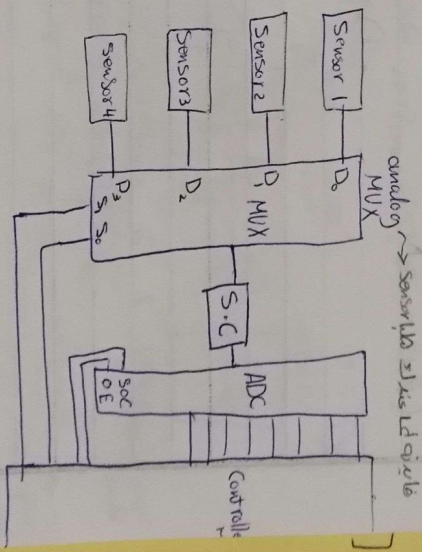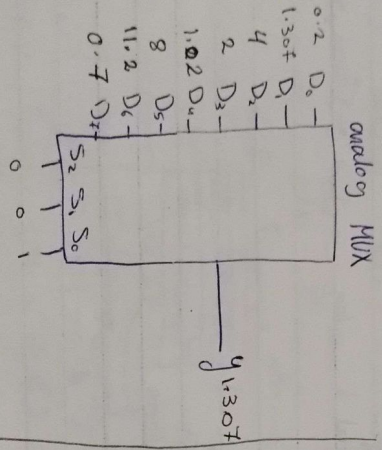TTL
 $5V \triangleq 1$
 $(2 \sim 5.5)$
 $0 \triangleq \text{Ground}$
 $(0 \sim 0.8)$



Agip آجيب

INTERNAL NOTES

Date

N


FROM

TO

Your Ref
Our Ref

Subject

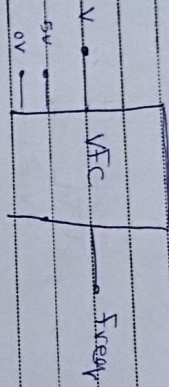Voltage to Freq Converter (VFC) AD method (2)



[10 KHz/V] \Rightarrow Rate "

(0V ~ 5V) \rightarrow Voltage Range


(0Hz ~ 50KHz) \rightarrow Freq Range

* Digital 1 analog 1 "مختلج" *
* "مختلج" *
* "مختلج" *

EX 1

Digital pulse

Counter

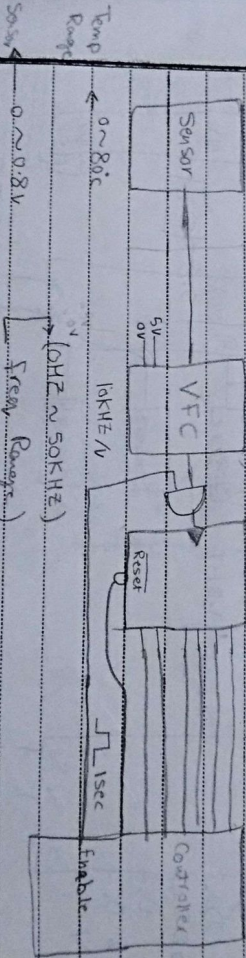


(a) 20°C \Rightarrow 0.2V \rightarrow 0.2V \times 10 KHz/V $=$ 2 KHz

What's o/p of counter	Exam Q
@47°C	10mV/°C
@47°C → 47V	0.47 × 5KHz = 2.35KHz
	470 Pulse

20/11/2019

EE463

(13)

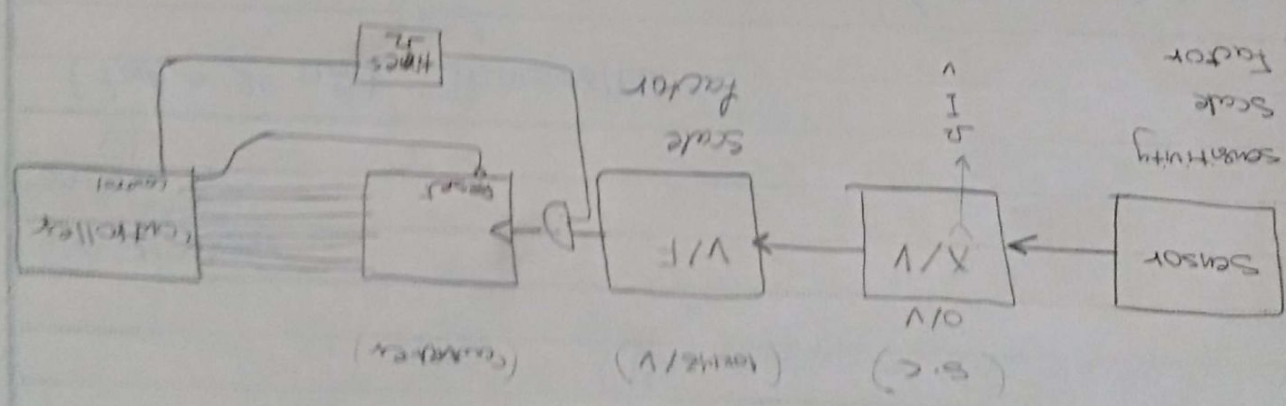

34 EX ▶ Using LM35 for the Range (30 ~ 90°C) and using (V/F) with Scale factor (3KHz/V) calculate :

- (a) Sensor o/p Range
V/F o/p Range
Counter o/p Range (using 0.2% duration)
- (b) what is the digital o/p of the counter if the Temperature is 68.2 °C
o/p (counter) is (00101101)₂ ≡ (237)₁₀
Temp Range (30 ~ 90°C)
Sensor o/p Range (30 × 10mV) ~ (90 × 10mV)
(0.3V ~ 0.9V)
- (c) what is the Value of Temperature if 5V digital V/F o/p Range (0.3V × 3KHz ~ 0.9V × 3KHz)
(0.9KHz ~ 2.7KHz)

MM

آجیب AgiP INTERNAL NOTES		Date	N
FROM	TO I wish I can sleep 3	Your Ref	Our Ref


Subject

Counter o/p Range (0.9 KHZ $\times 0.2\%$ ~ 2.7 KHZ $\times 0.2\%$)
 (180 pulse ~ 540 pulse)

(b) 409.2 Pulse


(c) 39.5°C

(4mA \sim 20 mA) Transmitter:

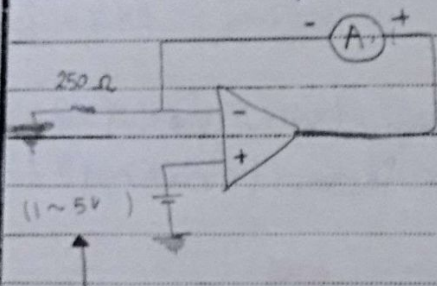


Current \rightarrow Data \rightarrow ~~...~~


(o/p of Sensor)

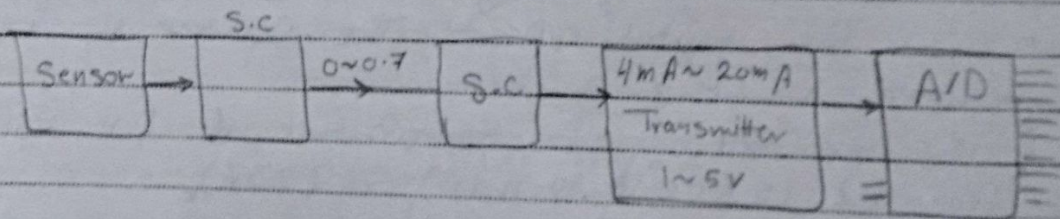

EX ▶

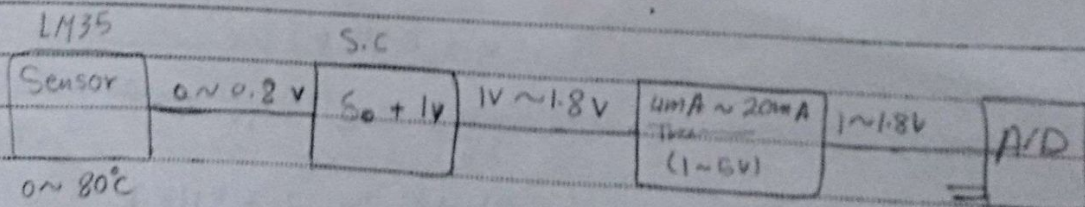

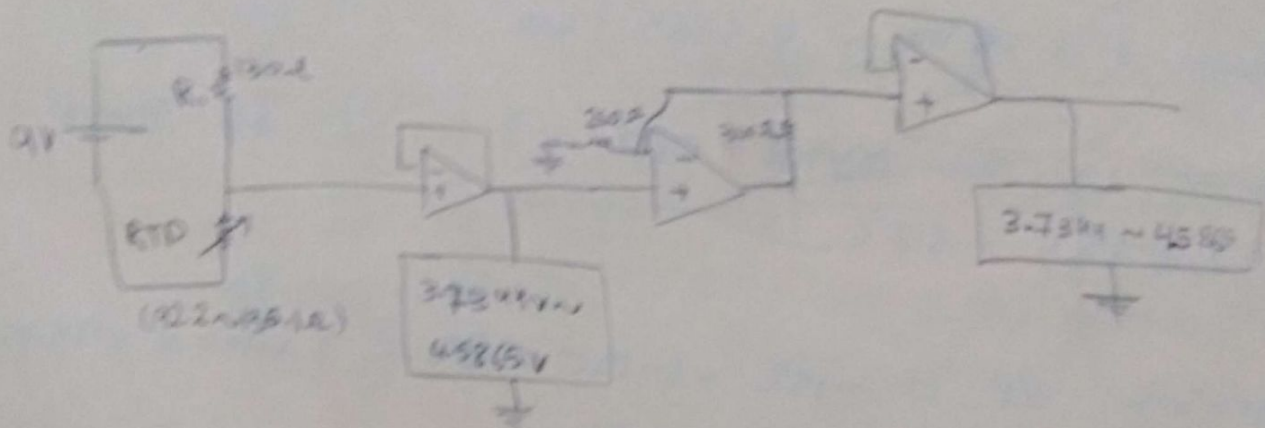* EX: using RTD PT100 for Temp Range $(-20^{\circ} \sim 90^{\circ})$
 in Voltage Divider with $R_1 = 130 \Omega$ design circuit
 to get the Temperature information for
 long distance to ADC with Voltage Reference (± 2) V



Solution: Temp Range $(-20^{\circ} \sim 90^{\circ})$

$$\text{sensor O/P } [100 + (0.39 \times -20^{\circ})] \sim [100 + (0.39 \times 90)]$$

$$(92.2 \Omega \sim 135.1 \Omega)$$

Voltage divider O/P Range

$$\text{at } -20^{\circ} \rightarrow V_0 = 9 \times \frac{92.2}{92.2 + 130} = 3.7544 \text{ Volt}$$

$$\text{at } -90^{\circ} \rightarrow V_0 = 9 \times \frac{135.1}{135.1 + 130} = 4.5865 \text{ Volt}$$

$$\begin{aligned} -2 &= 3.7544 M + \text{offset} \\ +2 &= 4.5865 M + \text{offset} \\ \hline 4 &= M \end{aligned}$$

$$M = 4.6943$$

(1)

$$\text{offset} = -19.5308$$

$$V_o = 4.6943 V_i - 19.5308$$

$$V_o = 4.6943 (V_i - 4.1655)$$

V_i	3.7344	4.1655	4.5865
V_o	-2.009	0	1.9994

Range (3.7344 ~ 4.5865) volt

if Temp

(A) what is The digital o/p of
is -15°C , 67°C .

Solution (A):

$$\text{Sensor o/p at } -15^\circ\text{C} = (-15^\circ\text{C} \times 0.39 \frac{\Omega}{^\circ\text{C}}) + 100 \Omega = 94.15 \Omega$$

$$\text{Voltage Divider o/p} = 9 \times \frac{94.15 \Omega}{130 + 94.15} = 3.78022 \text{ V}$$

$$\text{Transmitter o/p} = 3.78022 \text{ (because in The Range)}$$


$$\text{S.C. O/P} = (3.78028 - 4.1655) 4.6943 = -1.78509 \text{ V}$$

$$\Delta V = \frac{2 - (-2)}{2^8} = 0.015625 \text{ V}$$


$$\text{Digital o/p} = \frac{\text{Analog i/p} + V_{out}}{\Delta V}$$

$$= \frac{-1.78509 + 2}{0.015625}$$
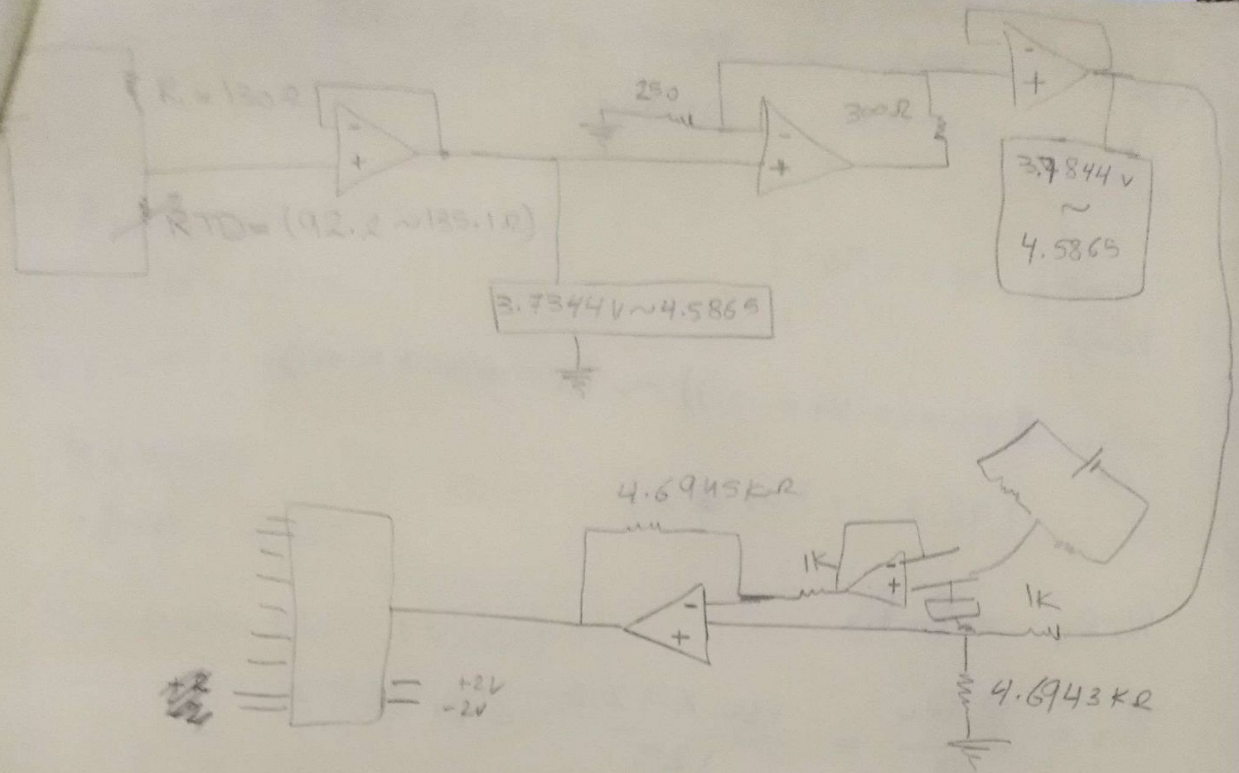
$$= 13.75 \simeq 13 \rightarrow (00001101)_2$$



(B)

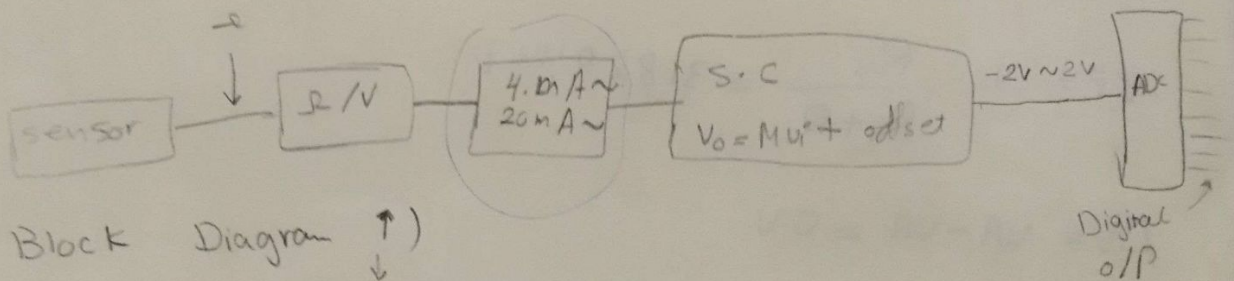

(Block Diagram ↑)
↓
سولت گیت لیک دیو
(B) ۹۷۷۷۷۷

(2)

at EX: Same as previous ex but using
Wheatstone bridge.

Solution:

Temp $(-20^{\circ}\text{C} \sim 90^{\circ}\text{C})$

Range

Sensor
o/p $((100 + (0.39 \times -20)) \sim (100 + (90 \times 0.39)))$
 $(92.2 \sim 135.1 \Omega)$

$$R_1 R_4 = R_2 R_3$$

$$R_3 = \frac{R_1 R_4}{R_2} = \frac{130 \times 92.2}{125} = 95.888 \Omega$$

@ -20°C

$$V_B = V_s \frac{R_3}{R_1 + R_3} = 3.82044 \text{ V}$$

$$V_P = V_s \frac{R_4}{R_4 + R_2} = 3.82044 \text{ V}$$


$$\Delta V = V_A - V_B = 0 \text{ V}$$


@ 90°C

$$V_D = 9 \times \frac{135.1}{135.1 + 130} = 4.6747 \text{ V}$$

$$\Delta V = 0.8543 \text{ V.}$$

bridge Range $(0 \sim 0.8543 \text{ V})$

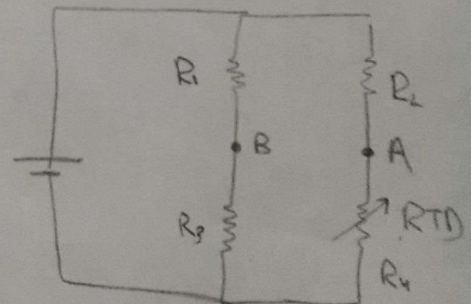

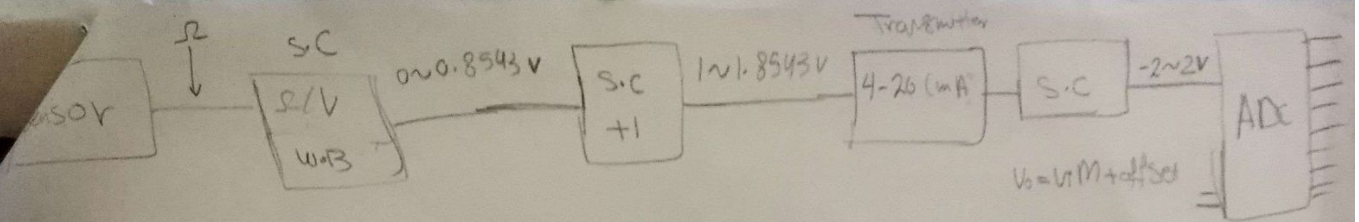

$$2 = 1.8543 M + \text{offset}$$

$$-2 = 1 M + \text{offset}$$

$$4 = 0.8543 M$$

$$M = 4.6821$$

$$\text{offset} = -6.682$$

$$V_o = 4.6821 (V_i - 1.42716)$$

25.01.18 Unit 16 Wheatstone bridge

lect in yellow paper


27/1/2019

lect (15)

Filters:

- low pass filter:

$$f_c = \frac{1}{2\pi RC}$$

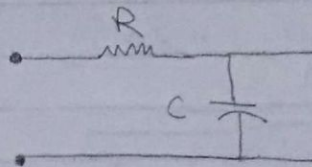

- Signal Freq: 1KHz, Noise: 1MHz ?

$$f_c = 2\text{KHz} \text{ or } 5\text{KHz} !!$$

$$V_o/V_i = \frac{1}{\sqrt{1 + \left(\frac{f_N}{f_c}\right)^2}} !!$$

38 EX ▶ The signal f_N Freq is 1KHz & undesired noise signal 1MHz. Design filter that attenuate the noise to 1%, and what is the effect of the filter on the desired signal?
Solution:-

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{f_N}{f_c}\right)^2}}$$

$$0.01 = \frac{1}{\sqrt{1 + \left(\frac{10^6}{f_c}\right)^2}} \Rightarrow f_c = 10000.5 \text{ Hz}$$

$$\text{The effect on the signal: } \frac{V_i}{V_o} = \frac{1}{\sqrt{1 + \left(\frac{f_s}{f_c}\right)^2}}$$

FROM

TO

Your Ref

Our Ref

Subject

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{1 \text{ kHz}}{10.5 \text{ Hz}}\right)^2}} = 0.99503 \Rightarrow 99.503\% \text{ from the signal.}$$

let $C = 0.1 \mu\text{F}$

$$R = \frac{1}{2\pi \times 10000.5 \times 1 \times 10^{-6}} = 159.146 \Omega$$

[160 Ω]

5% = 6%

1.0	1.1	1.2	1.3	1.4	1.5	1.6	1.8	2	2.2
2.4	2.7	3.0	3.3	3.6	4.3	4.7	5.1	5.6	6.2
6.8	7.5	8.2	9.1						

when $R = 160 \Omega$

$$f_c = \frac{1}{2\pi \times 160 \times 0.1 \times 10^{-6}} = 9947 \text{ Hz}$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{1000}{9947 \text{ Hz}}\right)^2}} = 0.99489 \Rightarrow 99.489\%$$

$\frac{1}{0.99489} = 1.005 \rightarrow$ Gain \star to Get back The Freq & all pervious Value

when $R =$

$$F_c = \frac{1}{2\pi \times 180 \times 0.1 \times 10^{-6}} = 8841.94 \text{ Hz}$$

$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{1000}{8841.94}\right)^2}} = 0.99366 \Rightarrow 99.366 \%$$

$$\text{Gain} = \frac{1}{0.99366} = 1.006 \checkmark$$

(16)

EE 463

30/1/2020

Signal freq 2 KHz, Noise 110 KHz at ^① [1% Noise attenuation.]

$$0.01 = \frac{1}{\sqrt{1 + \left(\frac{110 \text{ KHz}}{F_c}\right)^2}} \Rightarrow F_c = 1.105 \text{ KHz}$$

effect on the signal. $\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + \left(\frac{2 \text{ KHz}}{1.1 \text{ KHz}}\right)^2}} = 0.4819$

which is very bad

$\Rightarrow 48.19 \%$

②. up to 5% Noise attenuation.

TO

Our Ref

$$0.05 = \frac{1}{\sqrt{1 + \left(\frac{110 \text{ KHz}}{f_c}\right)^2}} - 5.5 \text{ KHz}$$

effect on the signal = 0.939 which is better "stronger"


③ up to 7% Noise attenuation

$$0.07 = \frac{1}{\sqrt{1 + \left(\frac{110 \text{ KHz}}{f_c}\right)^2}} = 7.71 \text{ KHz}$$

effect on The signal = 96.8%

$$\text{Gain} = \frac{1}{0.968} = 1.033$$

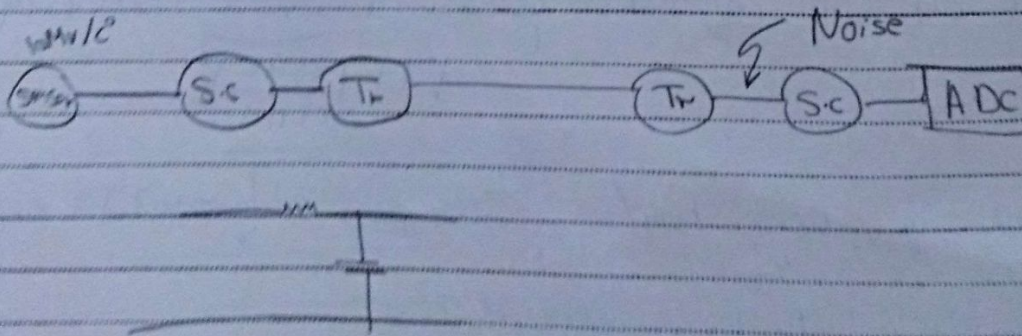
* when Noise attenuation up to 10%, $f_c = 11 \text{ KHz}$, effect = 98.38%



{3 iteration in exam}

High pass Filter $\rightarrow [F_s > F_c]$
 Low pass, High pass
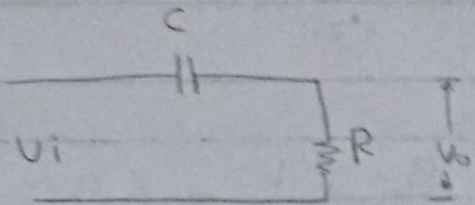
$$\frac{V_o}{V_i} = \frac{F/F_c}{\sqrt{1 + \left(\frac{F}{F_c}\right)^2}}$$



EX \rightarrow Noise 50 Hz, Signal 1 KHz (Select/design)
 The Filter Circuit & Calculate The effect on
 The Signal.

Solution :

$$0.01 = \frac{50 \text{ Hz} / F_c}{\sqrt{1 + \left(\frac{50}{F_c}\right)^2}} = 5 \text{ KHz} \rightarrow [\text{at } 1\%]$$

which is very bad because F_c is higher than
 The Signal.

[at 5%]

$$0.05 = \frac{50 \text{ Hz} / F_c}{\sqrt{1 + \left(\frac{50}{F_c}\right)^2}} = 998 \text{ Hz} \left[\begin{array}{l} \text{effect on The Signal} \\ 70\% \end{array} \right]$$

FROM

TO

Your Ref

Our Ref

Subject

(7)

3/2/2020

$$R = \frac{V}{I} = \frac{2.1}{10 \text{ mA}} = 6.90 \Omega$$

[Green = 2.1V]

$$R \approx 680 \Omega \rightarrow (2, 1, 0) \times 10^{-3}$$

[use 10mA] ✓
max 20mA

Q1 (18)

EXAM 1.2

6/2/2020


[B]

$$\text{Temp} = (-50^\circ\text{C} \sim 180^\circ\text{C})$$

$$\text{Sensor o/p Range} = [200 + (-50 \times 0.39)] \sim [200 + (180 \times 0.39)]$$

$$= 194.15 \Omega \sim 270.2 \Omega$$
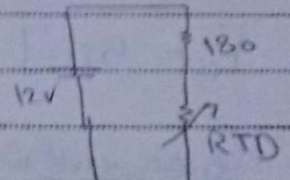
$$V_{\text{min}} = 12 \times \frac{194.15}{194.15 + 180} = 6.22691 \text{ V}$$



$$V_{\text{max}} = 12 \times \frac{270.2}{270.2 + 180} = 7.20218 \text{ V}$$

Voltage Divider o/p (6.22691 ~ 7.20218)

$$\text{Scale Factor} = 5 \text{ KHz} / 1.2 \text{ V} \Rightarrow 4.1667 \frac{\text{KHz}}{\text{V}}$$

$$\text{VFC output Range} (6.22691 \text{ V} \times 4.1667 \frac{\text{KHz}}{\text{V}} \sim 7.20218 \text{ V} \times 4.1667 \frac{\text{KHz}}{\text{V}})$$

$$(25.945458 \text{ KHz} \sim 30.008875 \text{ KHz})$$


$$20 \text{ Sample / Sec} \rightarrow \text{duty Cycle} = \frac{1}{20} = 0.05 \text{ Sec}$$

- Counter o/p Range: \rightarrow ~~1000~~

$$(0.05 \times 25.9454 \text{ KHz} \sim 0.05 \times 30.00875 \text{ KHz})$$

$$(1297.2729 \text{ pulses} \sim 1500.44375 \text{ pulses})$$

A

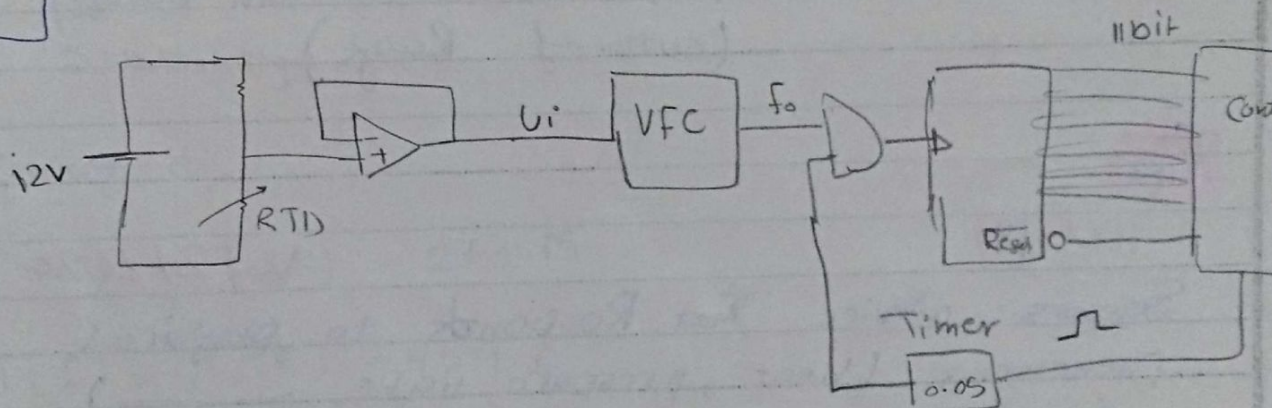

C

@ ~~112~~ 112°C

$$\text{Sensor o/p} : (112^\circ \times 2.39 \frac{^\circ}{^\circ}) + 200 = 243.68 \Omega$$

$$\text{VD o/p} = 12 \times \frac{243.68}{243.68 + 180} = 6.9018 \text{ V}$$

$$\text{VFC o/p} = 6.9018 \times 4.16667 = 28.7575$$

AgiP آجیب		INTERNAL NOTES	Date	N
FROM	TO		Your Ref	
			Our Ref	

Subject

$$\text{Counter o/p} = 28.757 \text{ KHz} \times 0.05 \text{ sec} \\ = 1437.877 = (1437)_{10}$$

$$(1011001101)_2$$

$$\boxed{d} \quad (1111101000)_2 \rightarrow (1000)_{10}$$


which is less than the min Range
(out of Range)

Q2

lect (9)

10/2/2020

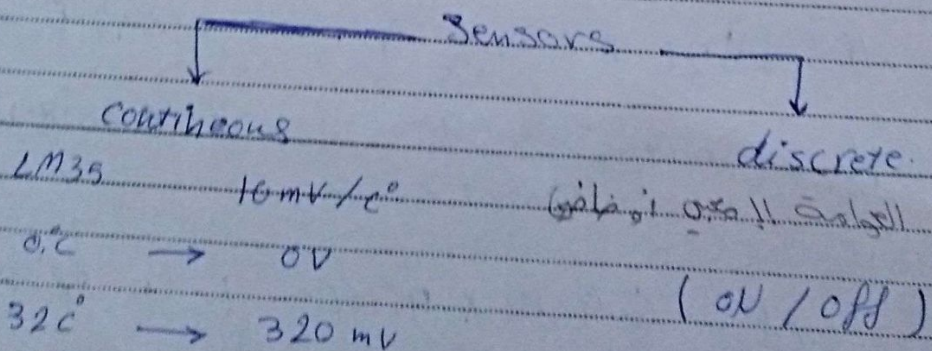Sensors: a device that responds to physical phenomena (heat, pressure, light, ...) and convert to signal relating to the quantity being measured.



1* passive sensor: R, L المستشعر السلبي

2* active sensor: solar cell المستشعر النشط

* Sensor Selection :

- o/p
- 1 Range , 2- Cost , 3- permability , 4- Reliability
5- linearity , 6- Response time , 7- Sensitivity
8- power consumption , 9- size , 10- Temp Range
11- Stability, 12 -

* Convert eq :

$$T(^{\circ}C) = T(K) - 273.15$$

$$T(^{\circ}F) = T(R) - 459.6$$

$$T(^{\circ}F) = \frac{9}{5} T(^{\circ}C) + 32$$

Rankine	Fahrenheit	Celsius	Kelvin
R°	F°	C°	K°
← 672 درجه رانكين	212	100	373
← 492 درجه رانكين	32	0	273

FROM

TO

Your Ref

Our Ref

Subject

Temperature:

PTC $T \uparrow$ O/P \uparrow

NTC $T \downarrow$ O/P \downarrow

PT has \sim sensitive $3.9^\circ\text{C}/\Omega$

($0.5 \sim 5$) \leftrightarrow RTD

($-100 \sim 135$)


بالقین

($-180 \sim 300^\circ\text{C}$)

نکلی

Gas Range

If my sensor not linear:

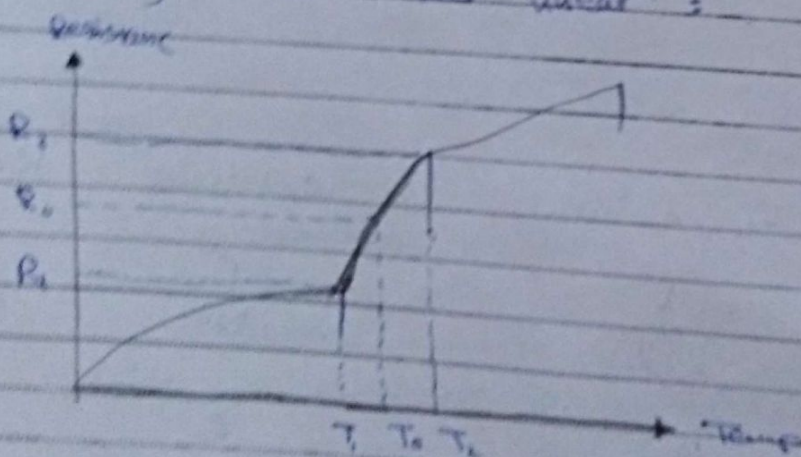

Linear approximation method ▶

$$R(T) = R(T_0) (1 + \alpha_0 \Delta T)$$

$$\Delta T = T - T_0$$

$$\alpha_0 = \frac{1}{R(T_0)} \frac{R_2 - R_1}{T_2 - T_1}$$

$R(T)$ approximation of Resistance at Temp T
 $R(T_0)$ " " " T_0

α_0 = fractional change in Resistance per degree of Temp.

lect(20)

13/2/2020

Ex: a Sample of metal Resistance versus Temperature has the following measured values.

	$T(^{\circ}F)$	$R(\Omega)$	
T_1	60	1060	R_1
	65	1076	
	70	1091	
T_0	75	1102	R_0
	80	1111	
	85	1117	
T_2	90	112.2	R_2

FROM

TO

Your Ref

Our Ref

Subject

Find the linear approximation of the Resistance Versus Temperature between 0 2, 90°F.

$$\alpha_0 = \frac{1}{R(T_0)} \left(\frac{R_2 - R_1}{T_2 - T_1} \right)$$

$$\alpha_0 = \frac{1}{110.2} \left(\frac{112.2 - 106.0}{90 - 60} \right) = 1.8753 \times 10^{-3}$$

$$T = 61^\circ\text{F}$$

$$R(T) = R(T_0) [1 + \alpha_0 \Delta T]$$

$$= 110.2 [1 + 1.8753 \times 10^{-3} (61 - 110.2)]$$

$$= 107.3068 \, \Omega$$

$$T = 65^\circ\text{F}$$

$$R(T) = 110.2 [1 + 1.8753 \times 10^{-3} (65 - 110.2)]$$

$$= 108.1334 \, \Omega \rightarrow$$

مفروضه 107.6

$$T = 87^\circ\text{F}$$

$$R(T) = 112.67 \, \Omega$$

$$\frac{107.1 - 106}{107.1} = 1\%$$

60°F is

$$107.1$$

نسبة الخطأ 1%

quadratic approximation. method :

~~Resistor~~ $R(T) = R(T_0) [1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2]$

$$\Delta T = T - T_0$$

$$\alpha_1 = \frac{1}{R(T_0)} \left(\frac{R_2 - R_1}{T_2 - T_1} \right)$$

Same as previous Ex using quadratic:

$$R(T) = R(T_0) [1 + \alpha_1 \Delta T + \alpha_2 (\Delta T)^2]$$

$$112.2 = 110.2 [1 + \alpha_1 (90 - 75) + \alpha_2 (90 - 75)^2]$$

$$106.0 = 110.2 [1 + \alpha_1 (60 - 75) + \alpha_2 (60 - 75)^2]$$

$$0.01814 = [\alpha_1 15 + 225 \alpha_2]$$

$$-0.03811 = [\alpha_1 15 + 225 \alpha_2]$$

$$\alpha_1 = 1.8667 \times 10^{-3}, \alpha_2 = -4.444 \times 10^{-5}$$

$$T = 61.5^\circ$$

$$R(T) = 106.36 \Omega$$

$$T = 87^\circ F$$

$$R(T) = 111.96 \Omega$$

$$T = 65^\circ F$$

$$R(T) = 107.65 \Omega$$

Agip

INTERNAL NOTES

Date

N

FROM

TO


Your Ref

Our Ref

Subject

Pect (21) 463

20/2/2020

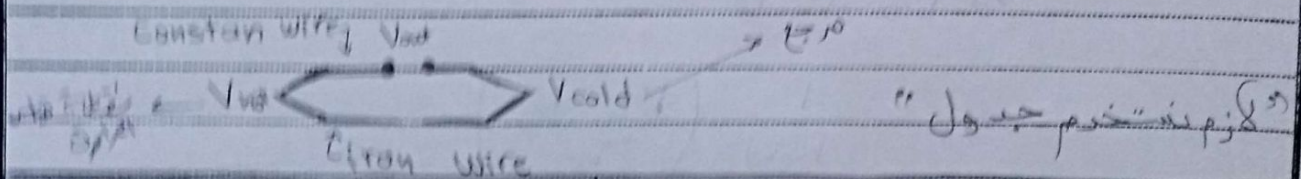Thermo Couple:
(جول) (جول)

Junction material	Range (°C)	nominal sensitivity (mV/°C)	Type
Platinum 90% / Rhodium	32 ~ 1800	7.7	B
Platinum 90% / Rhodium	0 ~ 2300	16	C
Platinum 90% / Rhodium	0 ~ 2300	16	C
chromel - Constantan	0 ~ 982	7.6	E
iron - Constantan	0 ~ 760	55	J
chromel - Alumel	184 ~ 126	39	K

1* Controlled Temperature reference block.

2 Reference Composition circuit

3 Software Reference Correction.

Composition

↑ *

* خرج المعجس بـ MV

* عند درجة 0°C

0 5 10 15 20 ~ ~ ~

-0 → الفوقيان يولد بالسالب

+0 → بالسوجب

J-Type

$$25^{\circ}\text{C} = 1.28 \text{ mV}$$

$$-30^{\circ}\text{C} = -1.48 \text{ mV}$$

$$675^{\circ}\text{C} = 37.6 \text{ mV}$$

$$-95^{\circ}\text{C} = -4.42 \text{ mV}$$

$$-125^{\circ}\text{C} = -5.61 \text{ mV}$$

$$-55^{\circ}\text{C} = -2.66 \text{ mV}$$

$$T_m = T_L + \left[\frac{T_H - T_L}{V_H - V_L} \right] (V_m - V_L)$$

$$V_m = V_L + \left[\frac{V_H - V_L}{T_H - T_L} \right] (T_m - T_L)$$

لما يكون الزخم من موجود في الجدول interpolation

EX: a Voltage of 23.72 mV is measured with K Thermo Couple, find The Temperature of measurement Junction :

$$\left. \begin{array}{l} V_L = 23.63 \\ T_L = 570^{\circ}\text{C} \end{array} \right\} \begin{array}{l} \text{أصغر من } V_m \\ T_m \end{array} \quad \left. \begin{array}{l} V_H = 23.84 \\ T_H = 575^{\circ}\text{C} \end{array} \right\} \begin{array}{l} \text{أكبر من } V_m \\ T_m \end{array}$$

FROM

10

Your Ref

Our Ref

Subject

$$T_m = 572.1429^\circ\text{C} \quad \checkmark \quad \text{Wavy equation}$$

EX: Find the voltage of Type J Thermocouple with zero degree reference if shield temp is -172°C

$$V_m = -7.18 \text{ mV}$$

$$T_m = -172^\circ\text{C}$$

$$V_H = -7.12 \text{ mV}$$

$$V_L = -7.27 \text{ mV}$$

$$T_H = 170^\circ\text{C}$$

$$T_L = 175^\circ\text{C}$$